

## Compensator Design:

Assume  $V_{osc}^{peak} = 1.8V$

$$TF = \frac{TF}{1.8}$$

Crossover frequency:  $f_{sw}$  in  $\frac{1}{10}$  to  $\frac{1}{5}$  range

Choose it  $\frac{1}{5}$  of the  $f_{sw} \Rightarrow f_{crossover} = 8kHz$

Location of pole and zeros:

$$f_{LC} = 918Hz$$

$$\frac{f_{sw}}{2} = 20kHz$$

$$f_{zer} > \frac{f_{sw}}{2} > f_{cross} > f_{LC}$$

Type 3-B

$$f_{zer} = 32.2kHz$$

$$f_{HPZ} = 17kHz$$

$$f_{cross} = 8kHz$$

At crossover freq

$$\phi_{osc} = -180^\circ$$

$45^\circ$  phase margin required

$$\text{Gain} = -5.46dB$$


$$\theta_{comp} = 45 - (-180) = 235^\circ$$

$$\text{Needed Gain} = 5.4dB = \underline{1.862 \text{ gain}}$$

①

IL method:
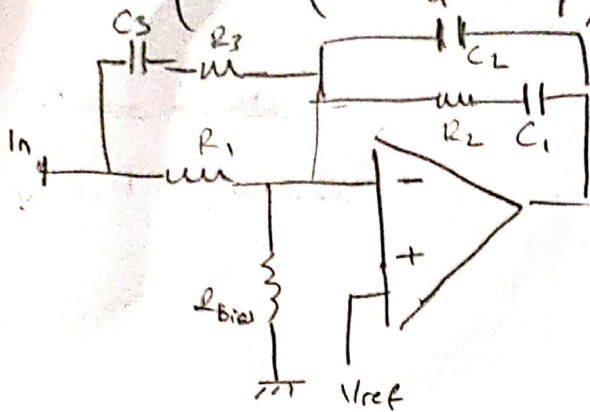
$$K = \left( \tan \left( \frac{\phi_{\text{comp}} + 90}{4} \right) \right)^2 = \underline{42.212}$$



$$R_1 = 1k \Omega$$

$$R_2 = \frac{1G(j\omega_{\text{crossover}}) | R_1}{\sqrt{K}} = \frac{1.862 \times 1000}{\sqrt{42.212}} = 286.59 \Omega \rightarrow 270 \Omega \text{ senkiler}$$

$$C_1 = \frac{\sqrt{K}}{2\pi f_{\text{crossover}} R_2} = \frac{\sqrt{42.212}}{2\pi(8000)(270)} = 478.96 \text{ nF} \rightarrow \underline{470 \text{ nF}}$$

$$C_2 = \frac{1}{2\pi f_{\text{cros}} R_2 \sqrt{K}} = \frac{1}{2\pi(8000)(270) \sqrt{42.212}} = 11.35 \text{ nF} \rightarrow 10 \text{ nF}$$

$$C_3 = \frac{\sqrt{K}}{2\pi f_{\text{cros}} R_1} = \frac{\sqrt{42.212}}{2\pi(8000) 1000} = 129 \text{ nF} \rightarrow \text{Bunu ne senkilerdir 6. levedim} \rightarrow 100 \text{ nF}$$

$$R_3 = \frac{1}{2\pi f_{\text{cros}} \sqrt{K} C_3} = \frac{1}{2\pi \times 8000 \times \sqrt{42.212} \times 100 \times 10^{-9}} = 326 \Omega \rightarrow 30 \Omega \text{ vardır}$$

(2)

$$V_{ref} = V_{out} \frac{R_{bias}}{R_{bias} + R_1}$$

$$2.17 = 17 \times \frac{R_{bias}}{1 + R_{bias}} \Rightarrow 200 \Omega = R_{bias}$$

$$\text{TF of compensator} = (s + 7.88 \times 10^3) \quad (s + 9.708 \times 10^3)$$

$$G(s) = - \frac{R_1 + R_3}{R_1 R_3 C_2} \times \frac{\left(s + \frac{1}{R_2 C_1}\right) \left(s + \frac{1}{(R_1 + R_3) C_3}\right)}{s \left(s + \frac{C_1 + C_2}{R_2 C_1 C_2}\right) \left(s + \frac{1}{R_3 C_3}\right)}$$

$$\downarrow$$

$$s \left(s + 3.783 \times 10^7\right) \left(s + 3.333 \times 10^7\right)$$

$$= - \frac{1030}{1000 \times 30 \times 10 \times 10^{-9}} = -0.00343 \times 10^9$$

$$G(s) = -0.00343 \times 10^9 \times \frac{(s^2 + 17.588 \times 10^3 s + 76.5 \times 10^6)}{s^3 + 7.116 \times 10^7 s^2 + 12.608739 \times 10^{10} s}$$